



# Electrical Power

# Quick recap

- The concepts of energy, work and power are the same across the range of physics
- Power is the rate at which energy is transferred
- Electrical power is the rate at which Electrical Potential (V) is transformed into
  - Light
  - Heat
  - Movement

# Consider our simple circuit

- With 5V electrical potential ...
- and a  $2\Omega$  resistance component ...
- 2.5A of current flows
- Power is given by the formula


$$P = VI$$

- with the units Watts (W)
- Thus the power available at the resistor is

$$P = VI = 5 \times 2.5 = 12.5W$$

Or

*12.5 Joules per second in energy terms*

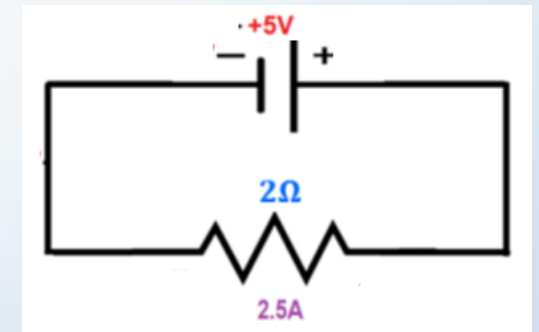

## This translates directly to ...

- Everything else you know about power and energy
- Consider a 1kg brick
- If you lift it 1m, you increase its  $E_p = mgh = 1 \times 9.8 \times 1 = 9.8J$
- Our previous circuit provides  $12.5Js^{-1}$ , thus if the resistor was an equivalent resistance motor ...
- It could raise the brick the 1m in  $\frac{9.8}{12.5} = 0.78s$

And ... that is exactly how electrical motors work

- The Wattage (W) of a motor is a measure of how much energy it puts out every second.
- Note a Kilowatt (kW) is 1000Watts(W) (kilo is '1000')
- Thus the term "kilowatt hours" (kWh) refers to how many kilowatts of energy will be produced over an hour
  - 4 kWh implies that 4kW is produced every hour

# A motor in a circuit

- Consider a simple motor circuit as shown on the right
- By Ohm's Law  $I = \frac{V}{R} = \frac{12}{8} = 1.5A$
- And  $P = VI = 12 \times 1.5 = 18W$
- So it can 'deliver'  $18J$  per second

